
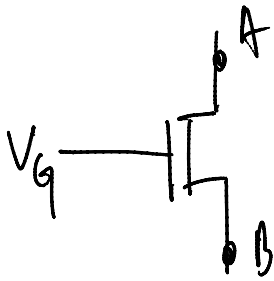


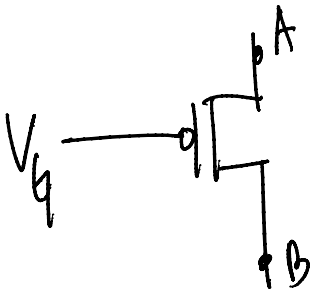CMOS - Complementary Metal Oxide Semiconductor




NMOS


$V_G = 1$, A and B is connected



PMOS

$V_G = 0$, A and B is connected.

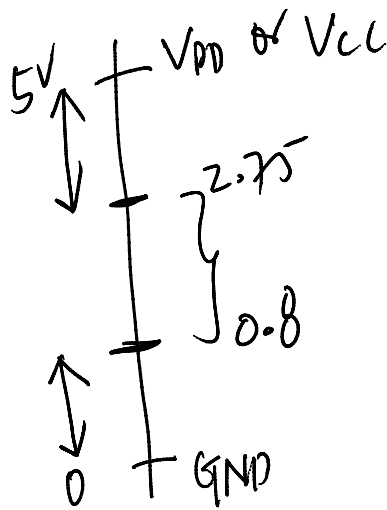

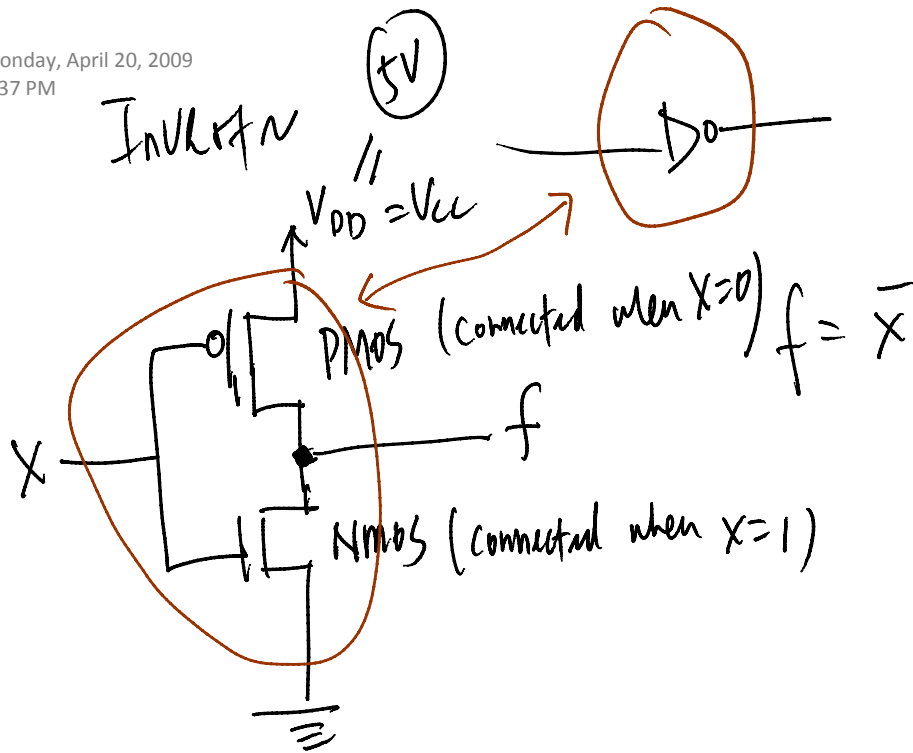

$X=0$, PMOS turn-on, NMOS turn-off, $f=1$


$X=1$, PMOS off, NMOS on, $f=0$

$$f = \bar{X}$$


↑
gates

$$f_1 = \overline{x_1 x_2}$$

2-input NAND gate

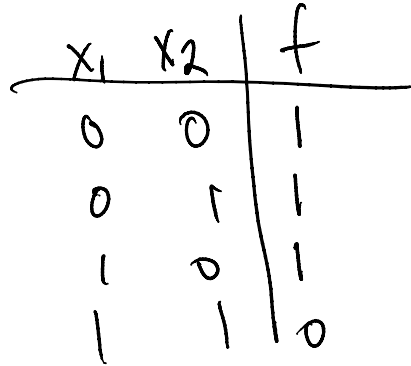


$$f = x_1 \cdot x_2$$

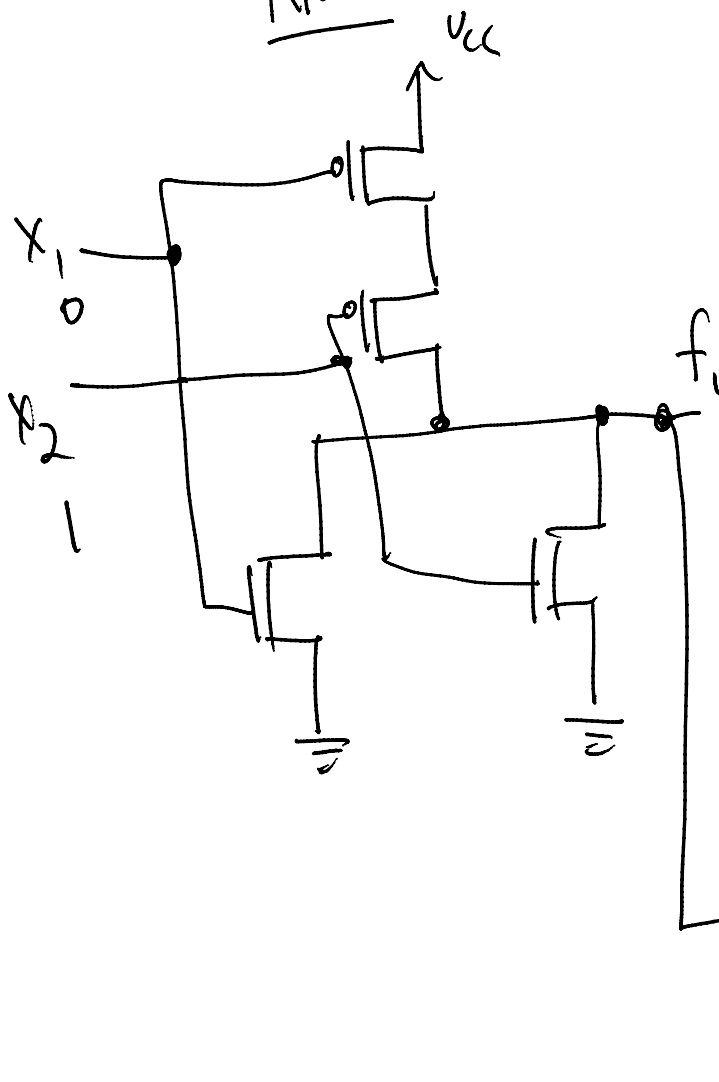Non

x_1	x_2	f_1
0	0	1
0	1	0
1	0	0
1	1	0

$$f_1 = \overline{x_1 + x_2}$$

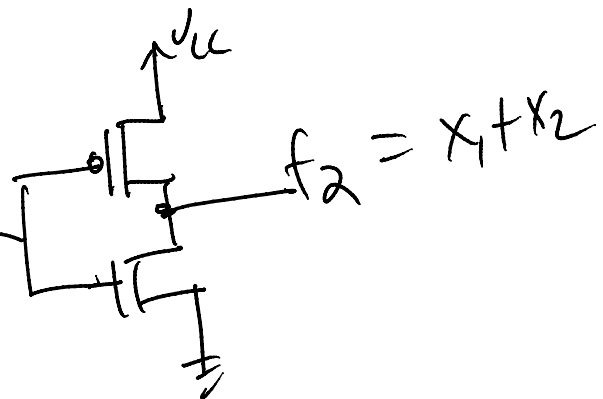

$$f_2 = x_1 + x_2$$

no overlap ! "110"

moore.

