

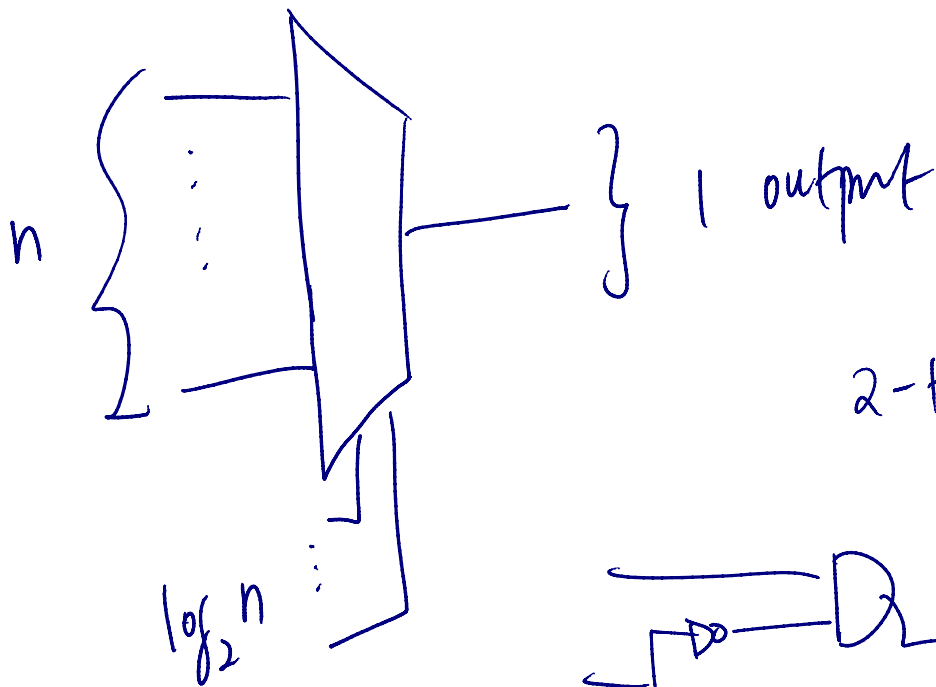


Multiplex

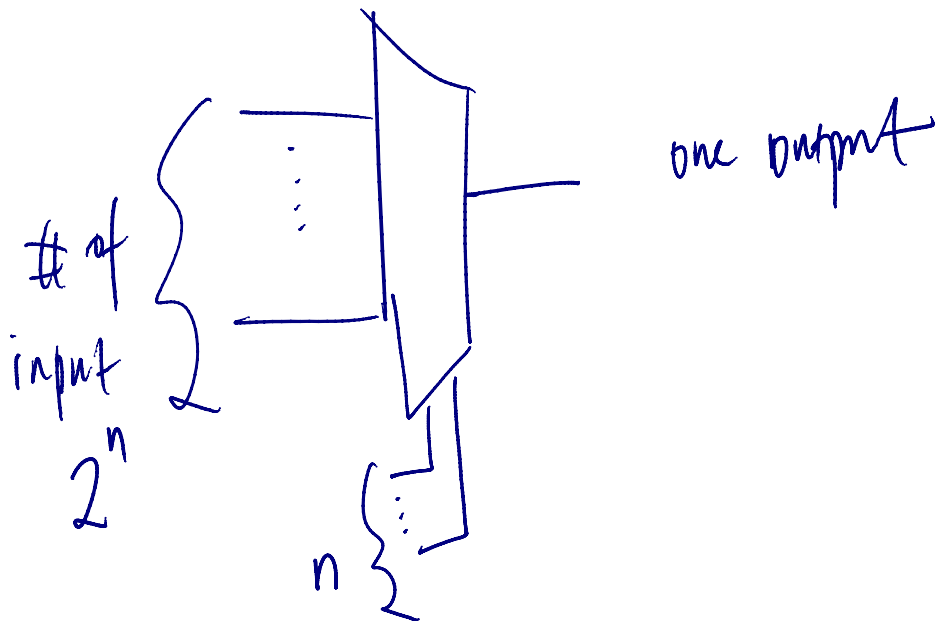





2-to-1

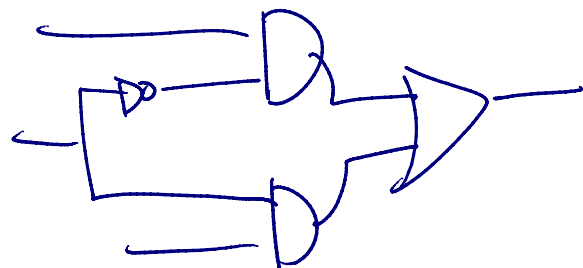

de-multiplex ✓


1 - 2 - 4

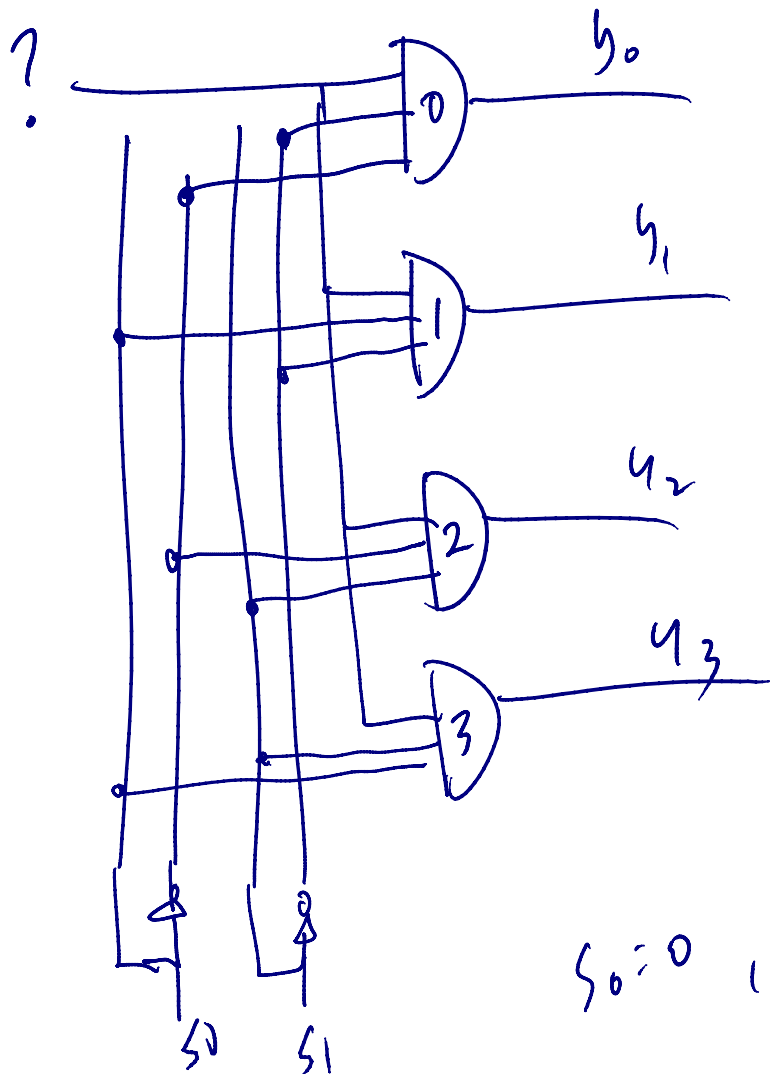

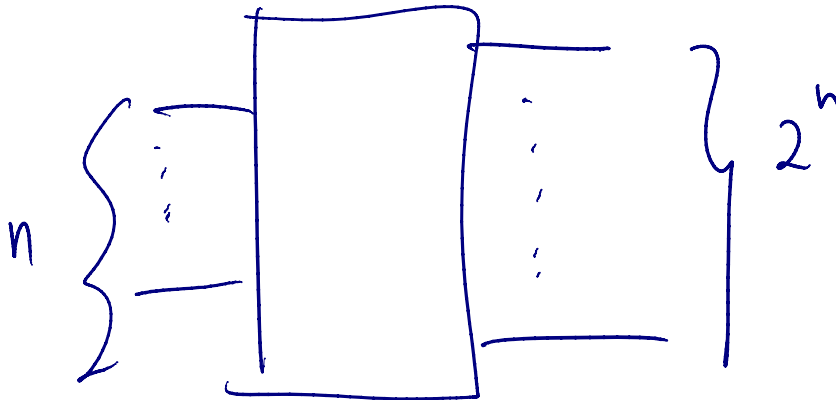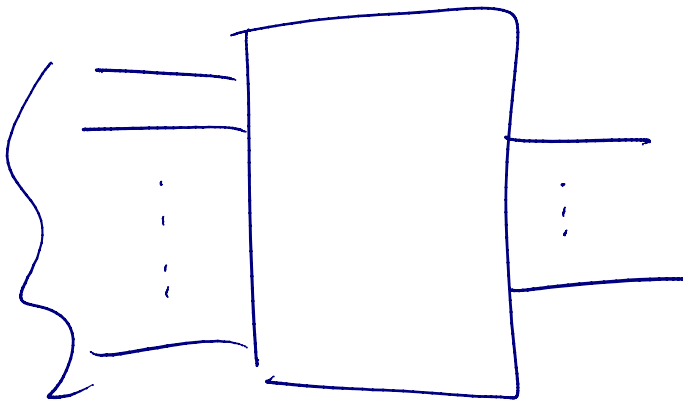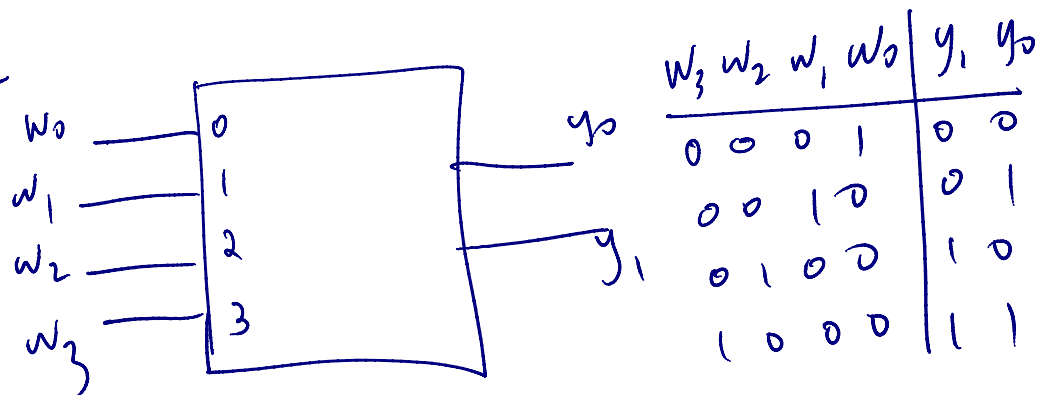decoderencoderencoder

decoder? when do I use it?

ROM
memory cells

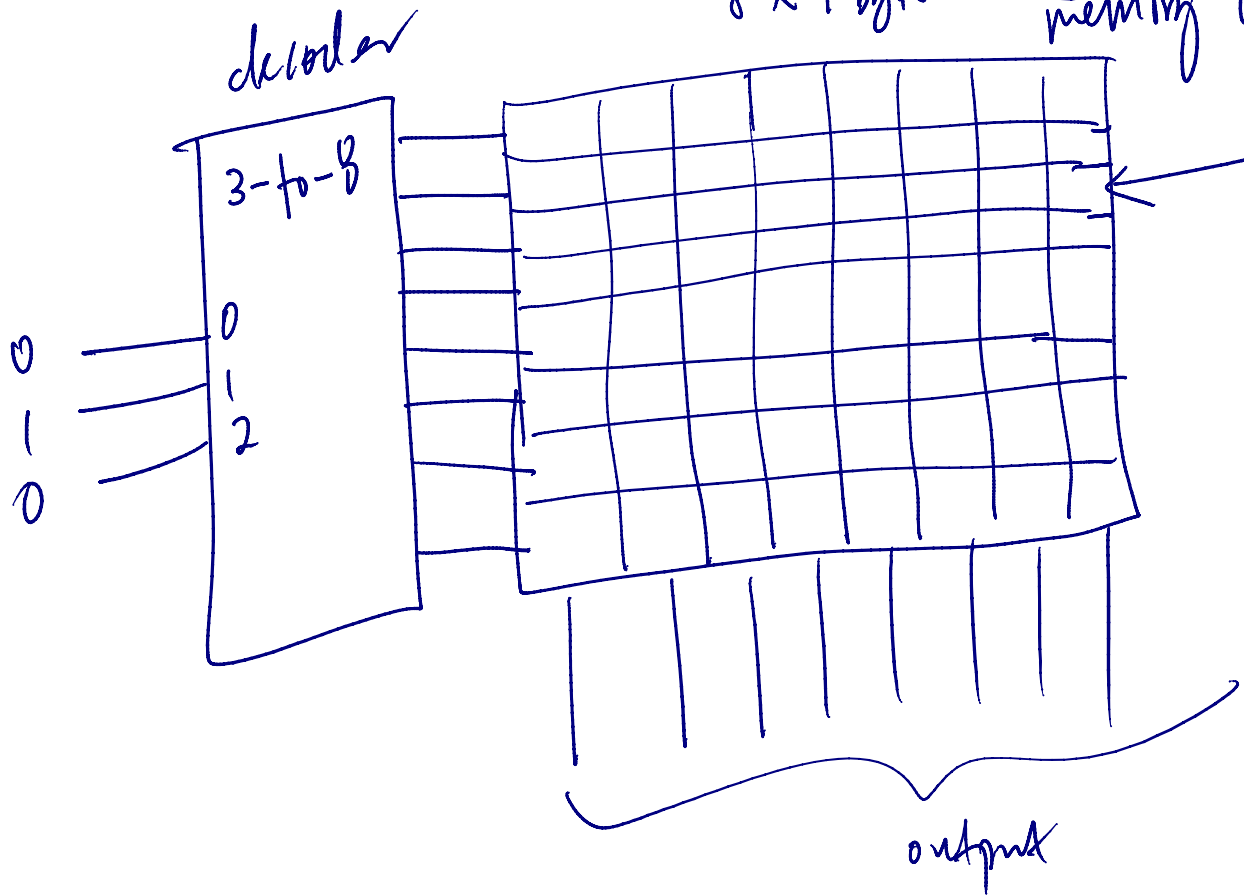

When?

4/6/2009

5/7

