

Boise State University
Department of Electrical and Computer Engineering
ECE 230 Digital Systems
Quiz 6 – October 8 2010

Name: key

- ④ Convert decimal number 14.875_{10} to binary representation with 4-bit accuracy.


$$\begin{array}{r} 8 \quad 4 \quad 2 \quad 1 \quad . \quad 0.5 \quad 0.25 \quad 0.125 \quad 0.0625 \\ 1 \quad 1 \quad 1 \quad 0 \quad . \quad 1 \quad 1 \quad 1 \quad 0 \end{array}$$

$$1110.1110_2$$

- ⑥ 2. Consider the function $f(x, y, z) = \sum m(1, 2, 3, 5, 6)$, where x is the MSB and y and the LSB. Use the true table to derive a circuit for f that uses a 2-to-1 multiplexer and some basic gates.

Note: Use Shannon's expansion, first variable to use is x , then y , then z .
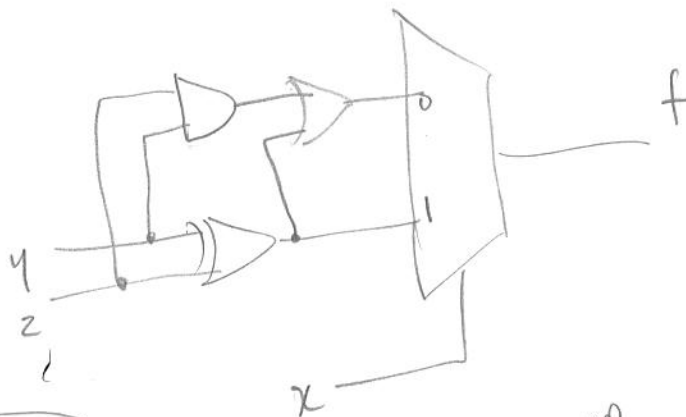
$$\begin{aligned} f &= \bar{x}\bar{y}z + \bar{x}y\bar{z} + \bar{x}yz + x\bar{y}z + xy\bar{z} \\ &= \bar{x}(\bar{y}z + y\bar{z} + yz) + x(\bar{y}z + y\bar{z}) \end{aligned}$$



Note:

$$\begin{aligned} &\bar{y}z + y\bar{z} + yz \\ &= (\bar{y} + y)z + y(\bar{z} + z) \\ &= z + y \end{aligned}$$

or

