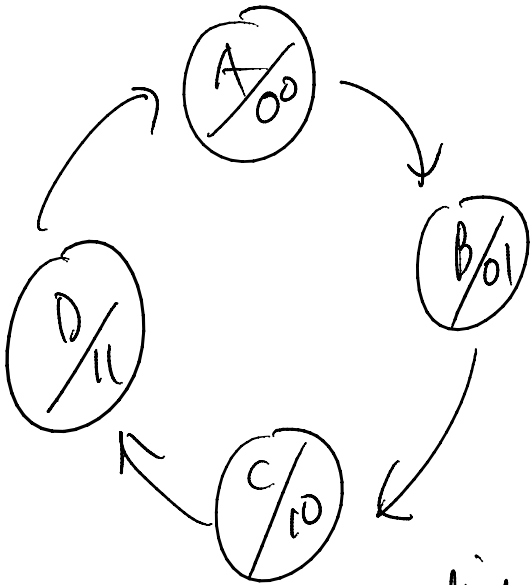


One-hot encoding!

Read Chapter 8 (21 - 30, 3) by wednesday




Present State	Next State	Output
A	B	00
B	C	01
C	D	10
D	A	11

encoding $A = "00", B = "01", C = "10", D = "11"$
 minimized bits encoding

one-hot encoding

$A = 0001$
 $B = 0010$
 $C = 0100$
 $D = 1000$

defect "01", overlapping

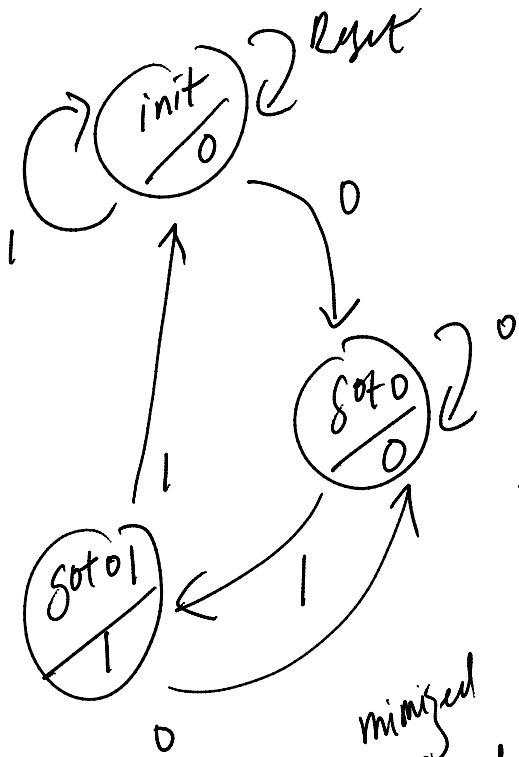

present state	Next state		output
	w=0	w=1	
init	goto 0	init	0
goto 0	goto 0	goto 01	0
goto 01	goto 0	init	1

init = "00", goto 0 = "01", goto 01 = "10"

Present state y ₂ y ₁ y ₀	Next state		output f
	w=0 y ₂ y ₁ y ₀	w=1 y ₂ y ₁ y ₀	
000	01	00	0
010	01	10	0
100	01	00	1

minimized
but
equality

one-hot encoding

init = "001"
goto 0 = "010"
goto 01 = "100"

Present state y ₂ y ₁ y ₀	Next state		output f
	w=0 y ₂ y ₁ y ₀	w=1 y ₂ y ₁ y ₀	
001	010	001	0
010	010	100	0
100	010	001	1