

5.8 using words with comm 1's comp

5.9 truth table

$$5.10 \quad C_k = x_k \oplus y_k \oplus S_k$$


$$S_k = ?$$



Add (half-adder, full-adder)

↑
cin


1-bit Adder \rightsquigarrow 4-bit adder

carry look adder

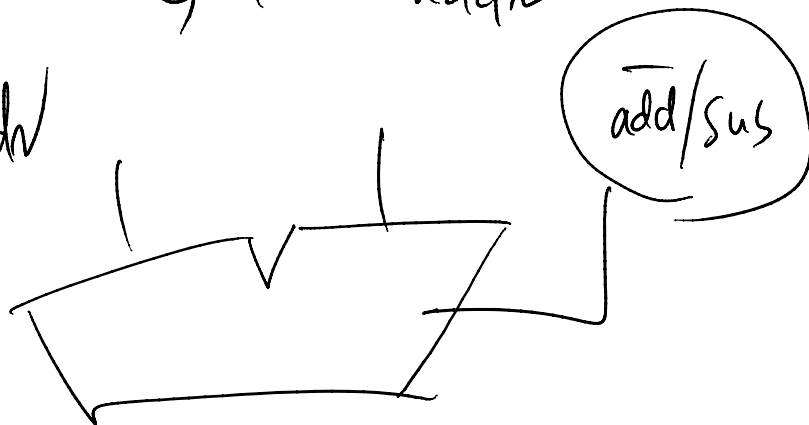


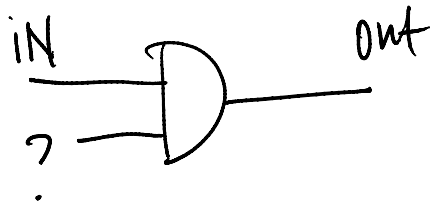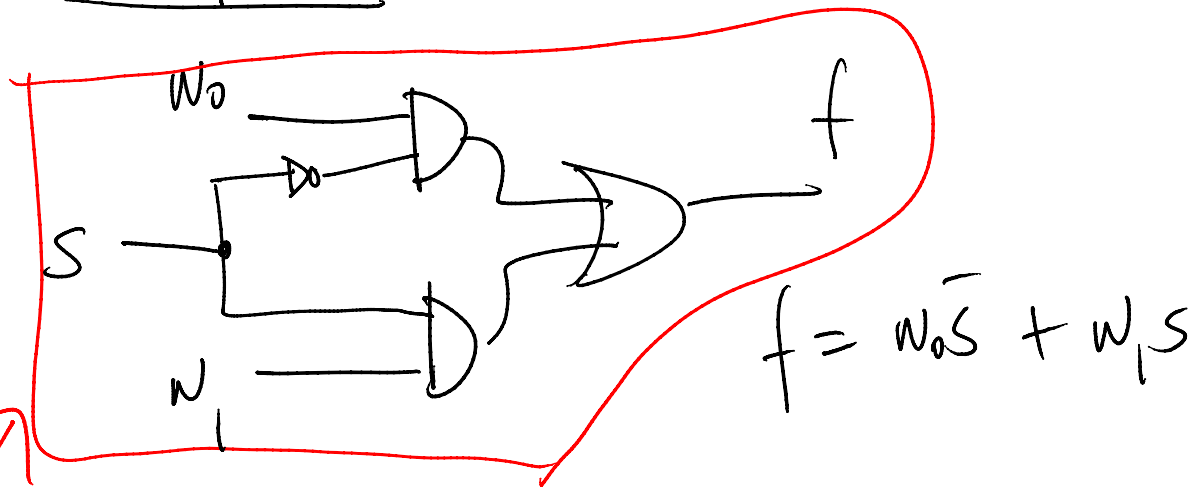Multiplexer
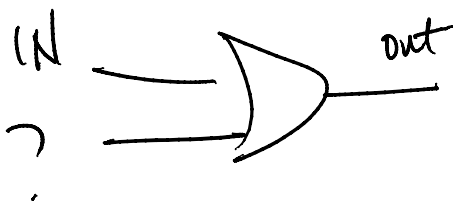
$$\begin{aligned} IN=0 &\Rightarrow out=0 \\ IN=1 &\Rightarrow out=? \end{aligned}$$


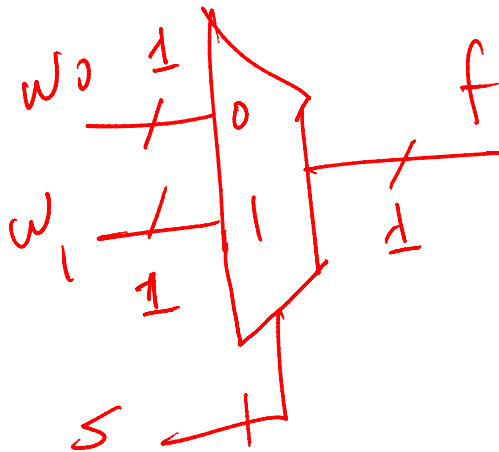
$$\begin{aligned} IN=0 &\Rightarrow out=? \\ IN=1 &\Rightarrow out=1 \end{aligned}$$




2-to-1 mux

s	f
0	w ₀
1	w ₁


2-to-1 mux

s	f
0	w_0
1	w_1



4-to-1 mux

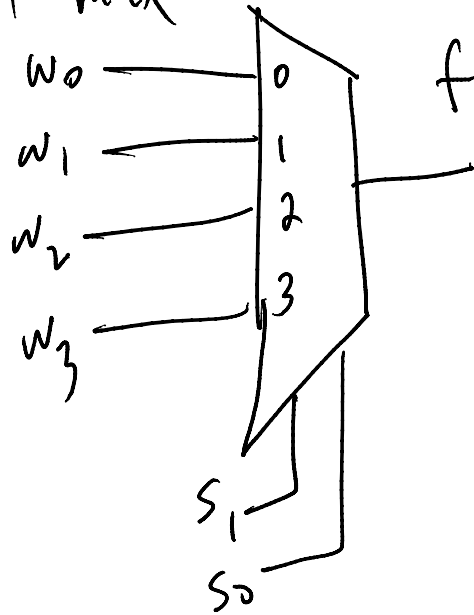

s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3

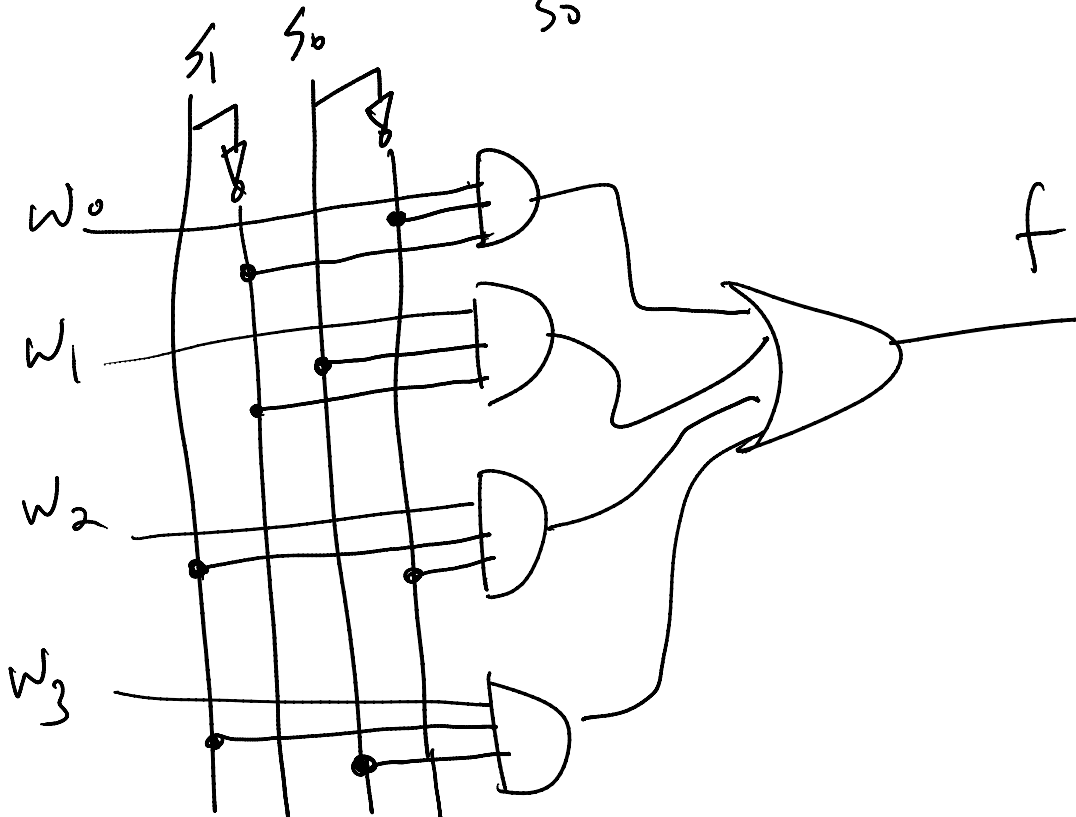

2-to-1 $\max(s)$ to build a 4-to-1 \max

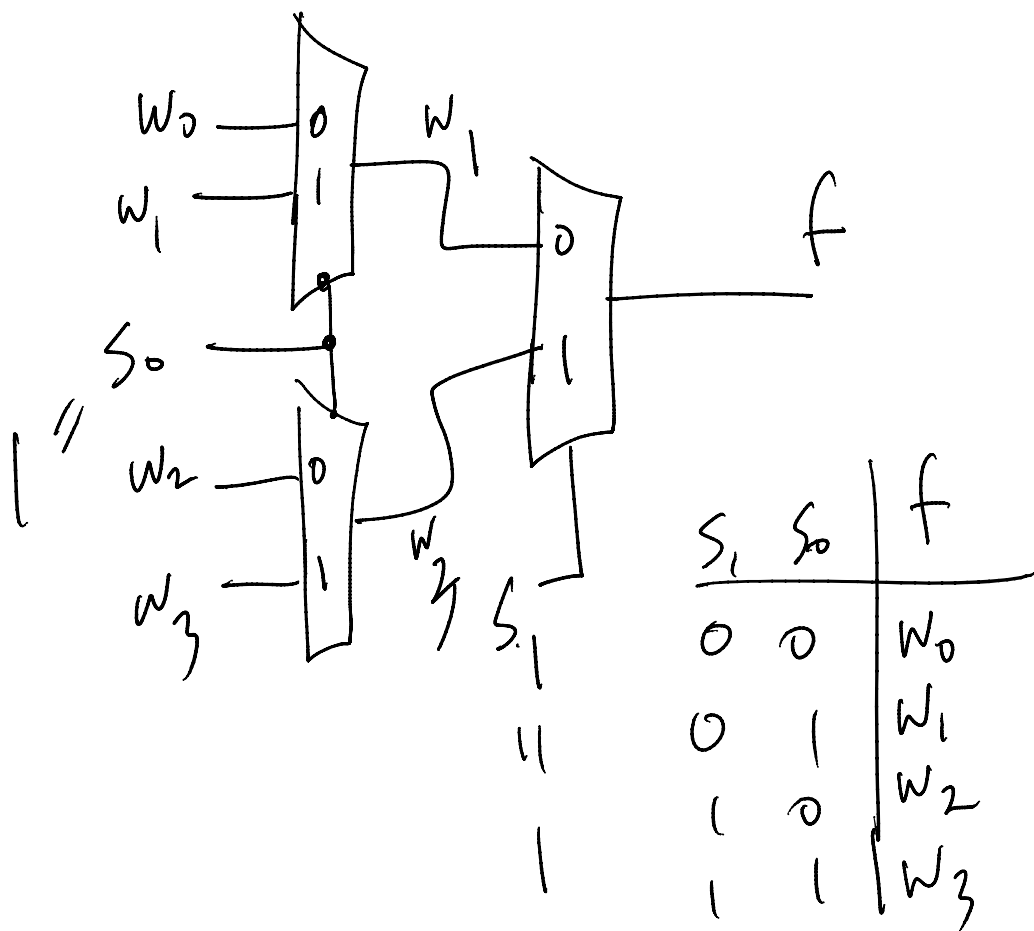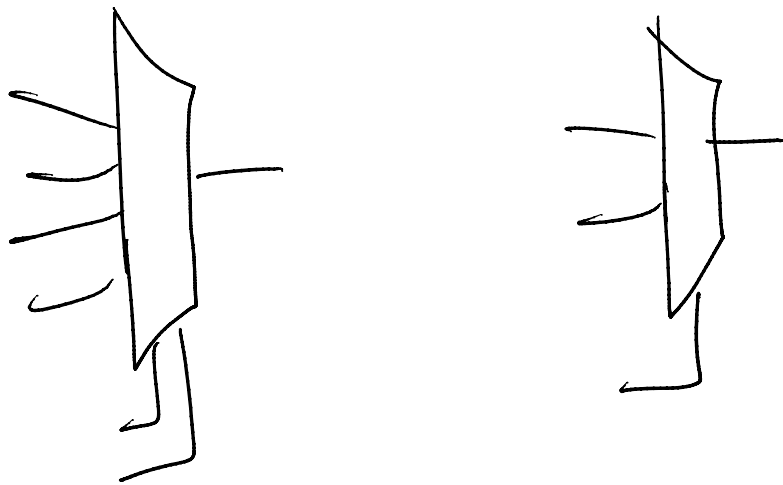

$$f = \bar{x}\bar{y}z + \bar{x}y\bar{z} + x\bar{y}\bar{z} + xy z$$