

Homework 1

Wednesday, August 25, 2010

11:39 PM

① Using AND, OR, and NOT gates, implement the following

$$f_1 = (x + y)z$$

$$f_2 = (x + y)(z + w)$$

$$f_3 = xy + zw$$

$$f_4 = \overline{xy} + \overline{zw}$$

② See section 2.4 of textbook for these questions:

What is logic synthesis?

What is logic analysis?

③ Using truth tables, show that Figure 2-10(a) has similar functionality to Figure 2-10(d). (see page 28 of textbook)

Homework 1 - cont

Wednesday, August 25, 2010
11:39 PM

Note for problem 3:

For each intermediate node, you should have a column in your truth table.

(4) using truth table to show that

(i) $x(y+z) = xy + xz$

(ii) $\overline{xy} = \overline{x} + \overline{y}$

(iii) $\overline{x+y} = \overline{x} \overline{y}$

(5) Find f_1 and f_2

